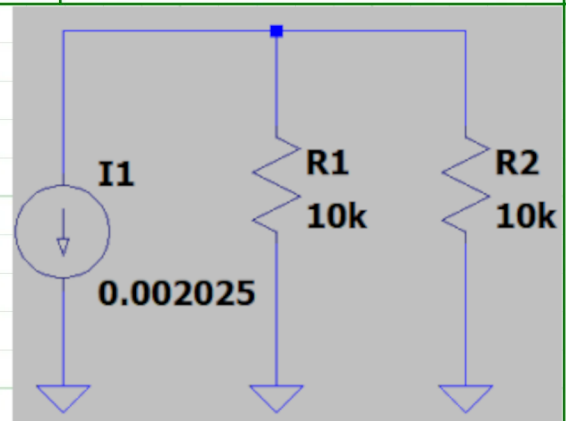


How much current flows in each resistor?

$$I_1 \cdot \frac{R_1}{R_1 + R_2} = \frac{1}{2} I_1 = 1.0125 \text{ mA}$$

Assuming that an NMOS is operating in the saturation region and a $k_p = \frac{100 \mu\text{A}}{\text{V}^2}$, $V_{GS} = 5\text{V}$ and $V_{th} = 0.5\text{V}$, find $\frac{W}{L}$ that generates an $I_D = 0.002025\text{A}$.



$$I_D = \frac{1}{2} k_p \frac{W}{L} V_{ov}^2$$


$$V_{ov} = 5\text{V} - 0.5\text{V} = 4.5 \rightarrow V_{ov}^2 = 20.25$$

$$\frac{2 \cdot (0.002025)}{20.25 \cdot 100 \mu\text{A}} = \frac{W}{L} = \textcircled{2}$$


Task 1 \rightarrow Replace I_1 w/ NMOS

... As shown, we can not. We need another source.

Literal interpretation

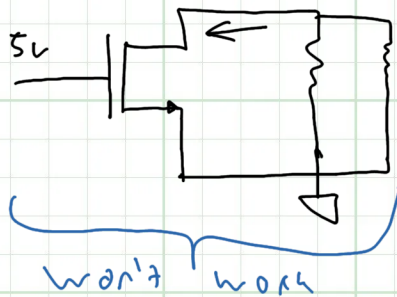


Possible Soln #1

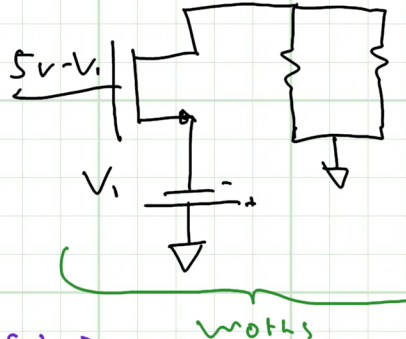

- + keeps resistors connected to gnd
- Charges V_1 to maintain V_{GS}
- 'Unusual' to have negative voltages in ckt

Possible Soln 2

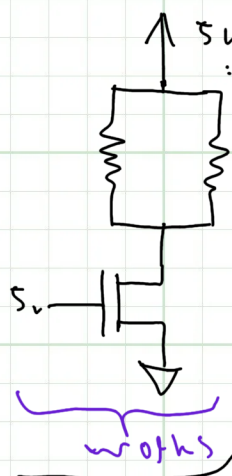

+ Simple, $R_D = R_1 \parallel R_2$

- Narrow window of operation $\rightarrow 4.5 \leq V_{DS} \leq 5$
 \hookrightarrow Caused by high gate voltage. Could pick non-5V V_{th}
- Resistors not gnd connected like in prelab

(Note that connecting the resistors to the source terminal is not a good idea - V_{GS} will change with different R_1, R_2 .)

Possible Soln 1 and 2 are mathematically identical \rightarrow just change defn of gnd.

I am choosing Soln 1 with $V_1 = -5\text{V}$